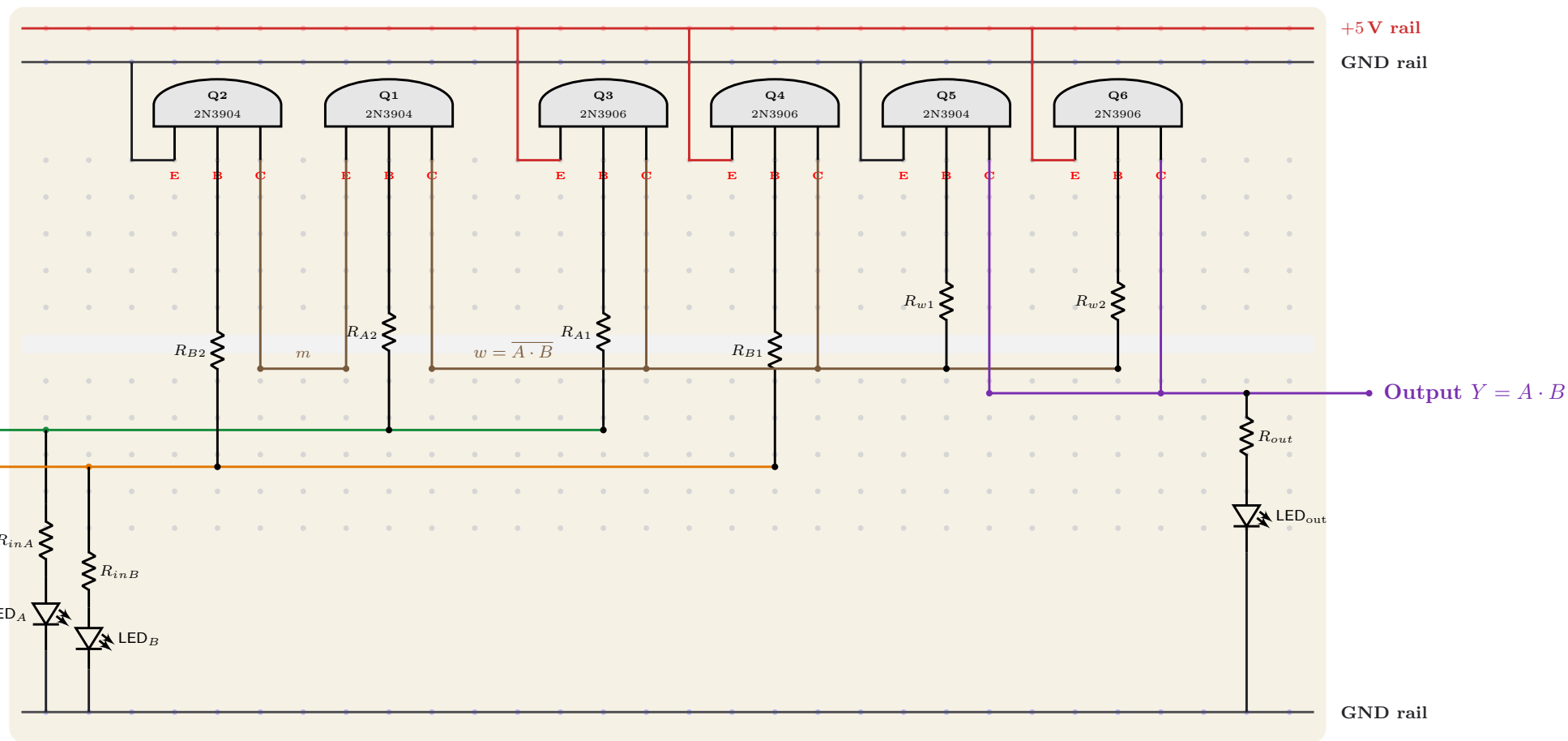




Jumper wires: — +5V — GND — A — B — m, w (internal) — output Y

Each column of five holes in a bank is one node; transistor legs are E B C in **adjacent** holes.

The two GND rails are **one node** – bridge them with a jumper at the board edge.